



American International University- Bangladesh (AIUB)
Faculty of Engineering

Course Name :	Electronic Devices	Course Code:	EEE 2013
Semester :	Summer 2019-20	Section:	N
Faculty :	NOWSHIN ALAM		



Assignment No :	3
Assignment Name :	CO3, CO4 (PO1: P.01.4.C3)

Student Name:	MOHAJMENUR RAHMAN	Student ID:	19-40338-1
---------------	-------------------	-------------	------------

Submission Date:	25.09.2020	Due Date :	25-09-2020
------------------	------------	------------	------------

Q-1

(a)

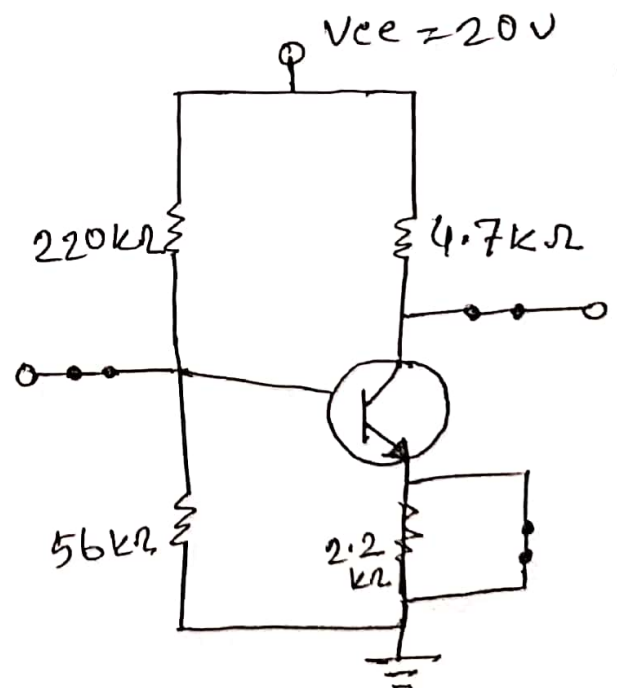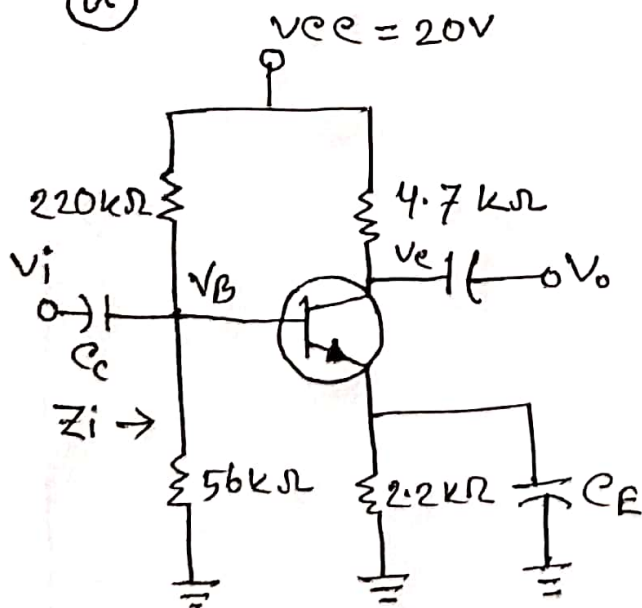

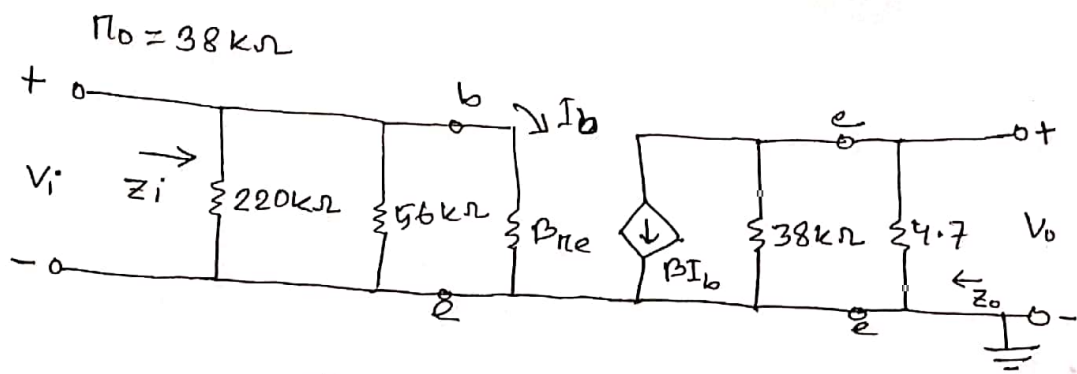


Fig: AC equivalent circuit

⑥

ID: 19-40338-1

$$V_{EE} = 20V$$

$$R_1 = 220k\Omega$$

$$R_2 = 56k\Omega$$

$$R_E = 4.7k\Omega$$

$$R_E = 2.2k\Omega$$

$$\beta = 38 \times 10 = 380$$

$$\pi_o = 38k\Omega$$

DC: Testing $\beta R_E > 10R_2$

$$380 \times 2.2 > 10 \times 56$$

$$836 > 560 \text{ (satisfied)}$$

using the approximate approach we obtain

$$\begin{aligned} V_B &= \frac{R_2}{R_1 + R_2} V_{EE} \\ &= \frac{56}{220 + 56} \times 20 \\ &= 4.057V \end{aligned}$$

$$V_E = V_B - V_{BE} = 4.057 - 0.7 = 3.357V$$

$$I_E = \frac{V_E}{R_E} = \frac{3.357}{2.2} = 1.525mA$$

$$\begin{aligned}
 r_e &= \frac{26 \text{ mV}}{I_E} \\
 &= \frac{26}{1.625} \\
 &= 17.049 \Omega
 \end{aligned}$$

$$\begin{aligned}
 \textcircled{c} \quad R' &= R_1 \parallel R_2 \\
 &= 200 \parallel 56 \\
 &= \frac{200 \times 56}{200 + 56} \\
 &= 44.637 \text{ k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 Z_i &= R' \parallel \beta r_e \\
 &= 44.637 \parallel (380)(17.049) \\
 &= 44.33
 \end{aligned}$$

$$\begin{aligned}
 Z_o &= R_e \parallel r_o \\
 &= 4.7 \parallel 38 = 4.18 \text{ k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 A_v &= \frac{R_e \parallel r_o}{r_e} \\
 &= \frac{4.18 \times 1000}{17.049} \\
 &= 245.18
 \end{aligned}$$

Ans.

Q-2

(a)

$$I_{DSS} = 38 \text{ mA}$$

$$V_p = -5 \text{ V}$$

V_{GS}	$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$
0	38 mA
-1	24.32 mA
-2	13.68 mA
-3	6.08 mA
-4	1.52 mA
-5	0 mA

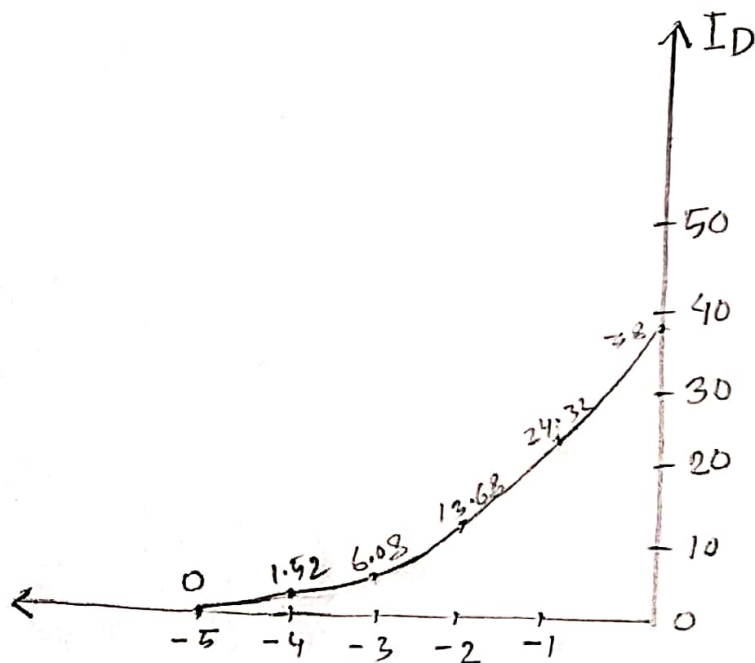


Fig: Transfer characteristic using Short-hand method.

6

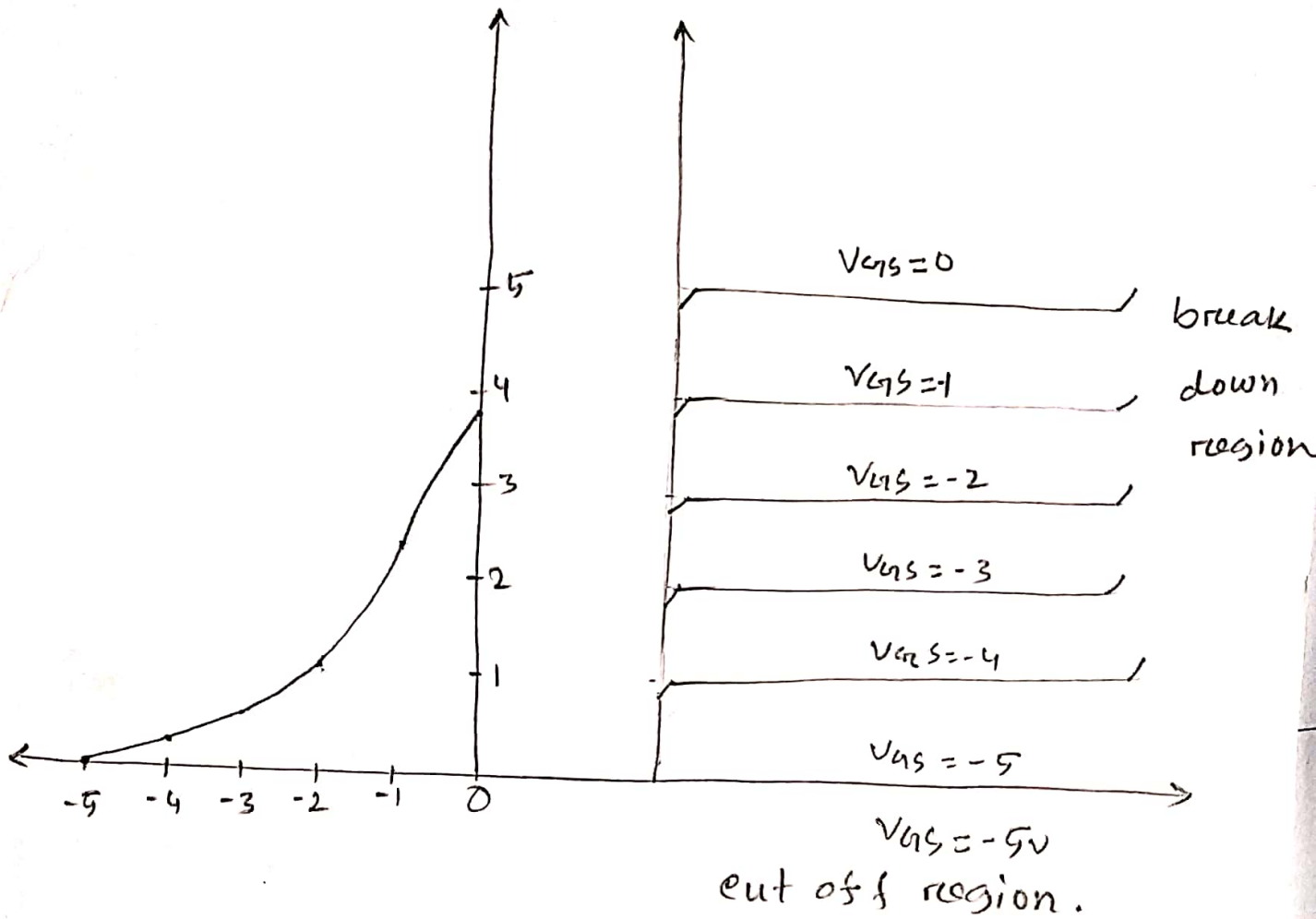


fig: Drain characteristics from the Transfer characteristics.

③ Max value of g_m

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$\begin{aligned} g_m &= \frac{-2 I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right) \\ &= -g_m \left(1 - \frac{V_{GS}}{V_P}\right) \end{aligned}$$

$$\begin{aligned} g_m &= \frac{2 I_{DSS}}{|V_P|} \\ &= \frac{2 \times 38 \times 10^{-3}}{|V_P|} \\ &= \frac{2 \times 38 \times 10^{-3}}{|5|} \\ &= 0.0152 \text{ ohm}^{-1} \end{aligned}$$

②

From ③


$$g_m = - \frac{2 I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P}\right)$$

$$V_{GS} = -3 \text{ V}$$

$$\begin{aligned} g_m &= \frac{-2 \times 38 \times 10^{-3}}{-5} \left(1 - \frac{(-3)}{(-5)}\right) \\ &= 6.08 \times 10^{-3} \text{ ohm}^{-1} \end{aligned}$$

Q-3

(a)

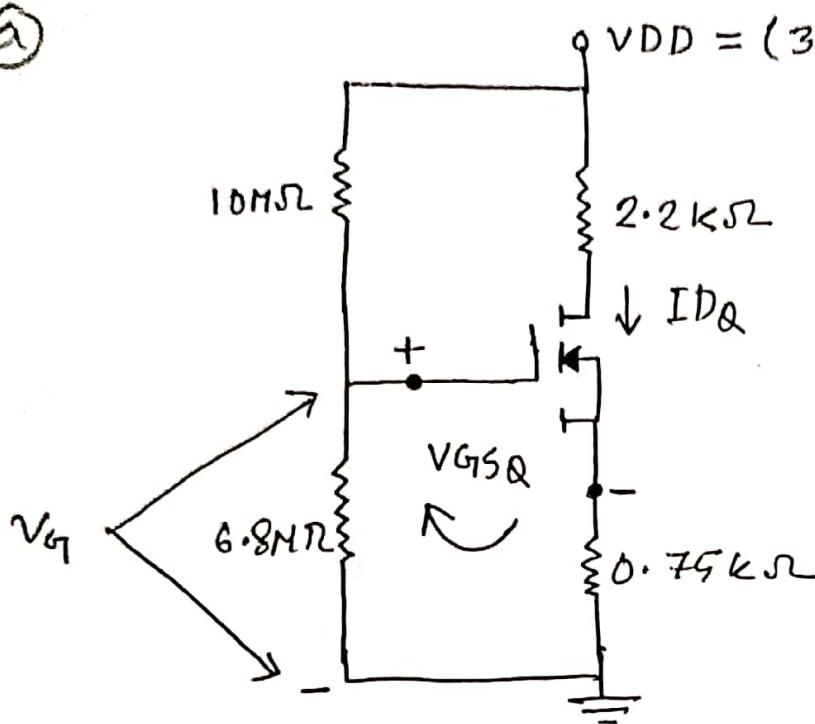

$$I_{D(on)} = 5 \text{ mA}$$

$$V_{GS(on)} = 6 \text{ V}$$

$$V_{GS(TH)} = 3 \text{ V}$$

$$R_1 = 10 \text{ M}\Omega, R_2 = 6.8 \text{ M}\Omega$$

$$R_D = 2.2 \text{ k}\Omega, R_S = 0.75 \text{ k}\Omega$$

$$V_G = \frac{R_2 \times V_{DD}}{R_1 + R_2} = \frac{6.8 \times 23.8}{10 + 6.8} = 9.63 \text{ V}$$

Applying KVL

$$V_G - V_{GS} - I_D R_S = 0$$

$$V_{GS} = V_G - I_D R_S$$

$$V_{GS} = 9.63 - I_D (750) \dots \dots (1)$$

We know

$$I_D = K (V_{GS} - V_T)^2$$

$$I_D = K (V_{GS} - 3)^2 \dots \dots (11)$$

Now

$$\begin{aligned}k &= \frac{I_{D(on)}}{(V_{GS(on)} - V_T)^2} \\&= \frac{5 \times 10^{-3}}{(6 - 3)^2} \\&= 5.56 \times 10^{-4} \text{ A V}^{-2}\end{aligned}$$

From eqn .. (ii)

$$I_D = 5.56 \times 10^{-4} (V_{GS} - 3)^2 \dots (iii)$$

From eqn (iii)

$$\text{Let } V_{GS} = 8 \text{ V}$$

$$\begin{aligned}I_D &= 5.56 \times 10^{-4} (8 - 3)^2 \\&= 13.9 \text{ mA}\end{aligned}$$

$$\text{Let } V_{GS} = 10 \text{ V}$$

$$\begin{aligned}I_D &= 5.56 \times 10^{-4} (10 - 3)^2 \\&= 27.24 \text{ mA}\end{aligned}$$


$$\text{Let } V_{GS} = 12 \text{ V}$$

$$\begin{aligned}I_D &= 5.56 \times 10^{-4} (12 - 3)^2 \\&= 45.03 \text{ mA}\end{aligned}$$

$$\text{Let } V_{GS} = 3 \text{ V}$$

$$\begin{aligned}I_D &= 5.56 \times 10^{-4} (3 - 3) \\&= 0\end{aligned}$$

The transfer characteristics curve

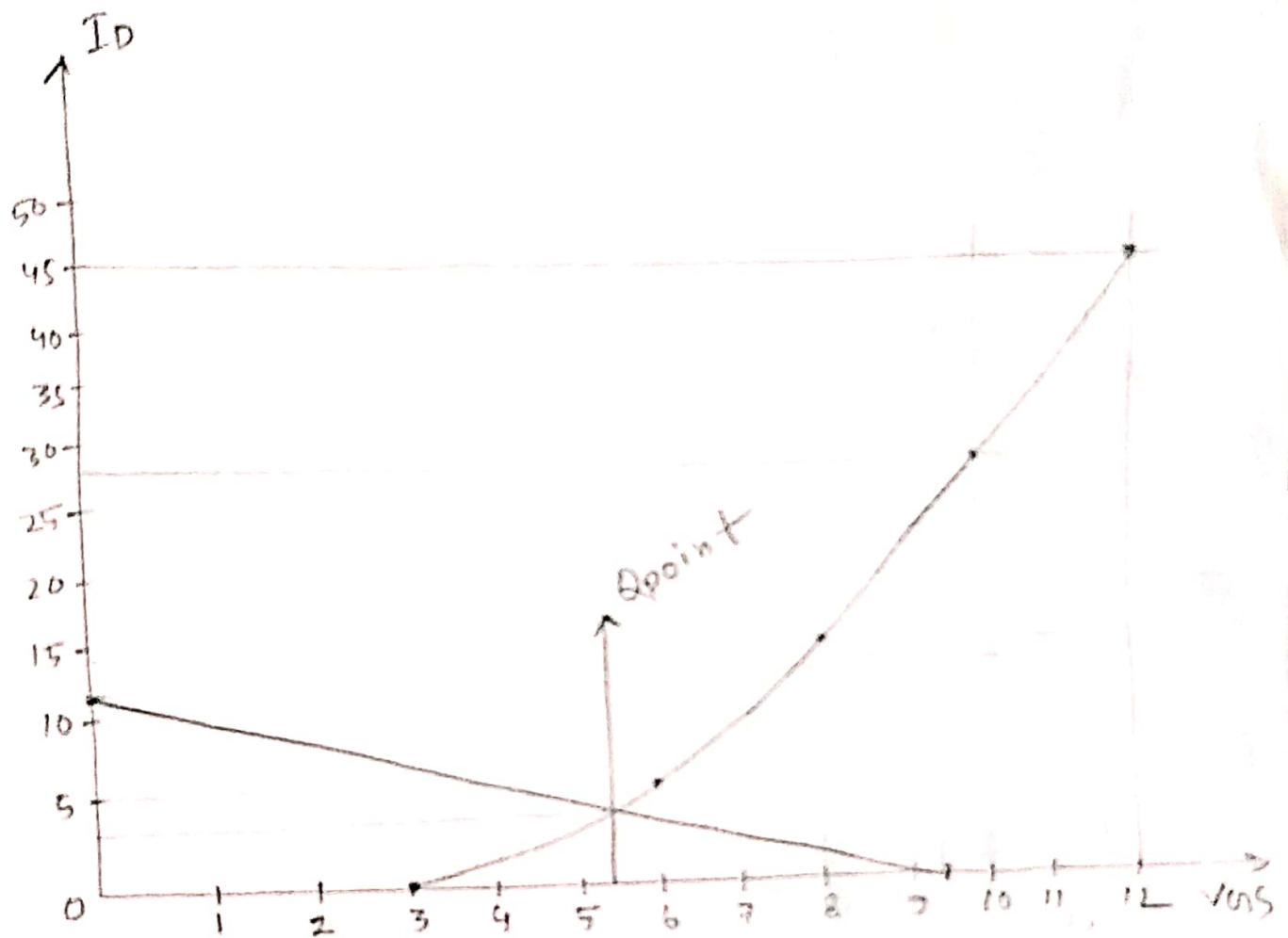

$$I_{DQ} = 5 \text{ mA}$$

$$V_{GSQ} = 5.2 \text{ V}$$

(b)

From eqn (1)

$$V_{GS} = 9.63 - I_D(750)$$

$$\text{let } I_D = 0$$

$$V_{GS} = 9.63$$

$$\text{let } V_{GS} = 0$$

$$I_D = \frac{9.63}{750} = 12.8 \text{ mA}$$

$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

$$= 23.8 - 3(2.2 + 0.75)$$

$$V_{DS} = 14.95 \text{ V.}$$

$$V_D = V_{DS} + V_S$$

$$\begin{aligned} V_D &= V_{DS} + V_S \\ &= 14.95 + 2.25 \\ &= 17.2 \end{aligned}$$

$$V_{GD} = V_{GS} - V_D$$

$$= 9.63 - 17.2$$

$$= -7.57 \text{ V}$$


$$V_S = I_D R_S$$

$$= 3 \times 0.75$$

$$= 2.25$$

Q-4

(a)

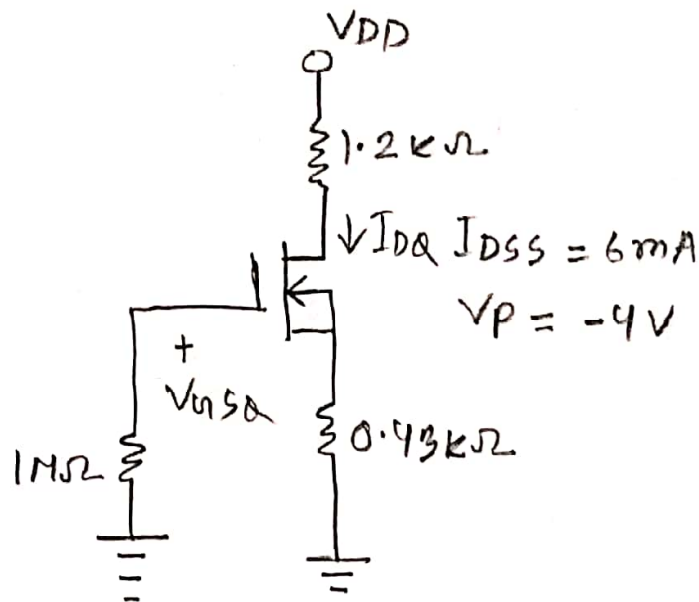

Applying KVL,

$$-V_{GS} - I_D R_S = 0$$

$$V_{GS} = -I_D R_S$$

$$= -I_D (0.43) \dots \textcircled{1}$$

Let's applying shorthand method

$$I_{DSS} = 6\text{mA}$$

$$V_P = -4\text{V}$$

1 \rightarrow if $V_{GS} = 0$

$$I_D = I_{DSS} = 6\text{mA}$$

2 \rightarrow if $V_{GS} = 0.3 V_P$

$$= 0.3 (-4)$$

$$= -1.2\text{V}$$

$$\begin{aligned}
 I_D &= \frac{I_{DSS}}{2} \\
 &= \frac{6}{2} \\
 &= 3
 \end{aligned}$$

$$\begin{aligned}
 3 \rightarrow \text{if } V_{GS} &= 0.5 V_P \\
 &= 0.5 (-4) \\
 &= -2
 \end{aligned}$$

$$I_D = \frac{I_{DSS}}{4} = \frac{6}{4} = 1.5$$

$$\begin{aligned}
 4 \rightarrow \text{if } V_{GS} &= V_P \\
 &= -4V
 \end{aligned}$$


$$I_D = 0$$

We know that

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$V_{GS} = 1V$$
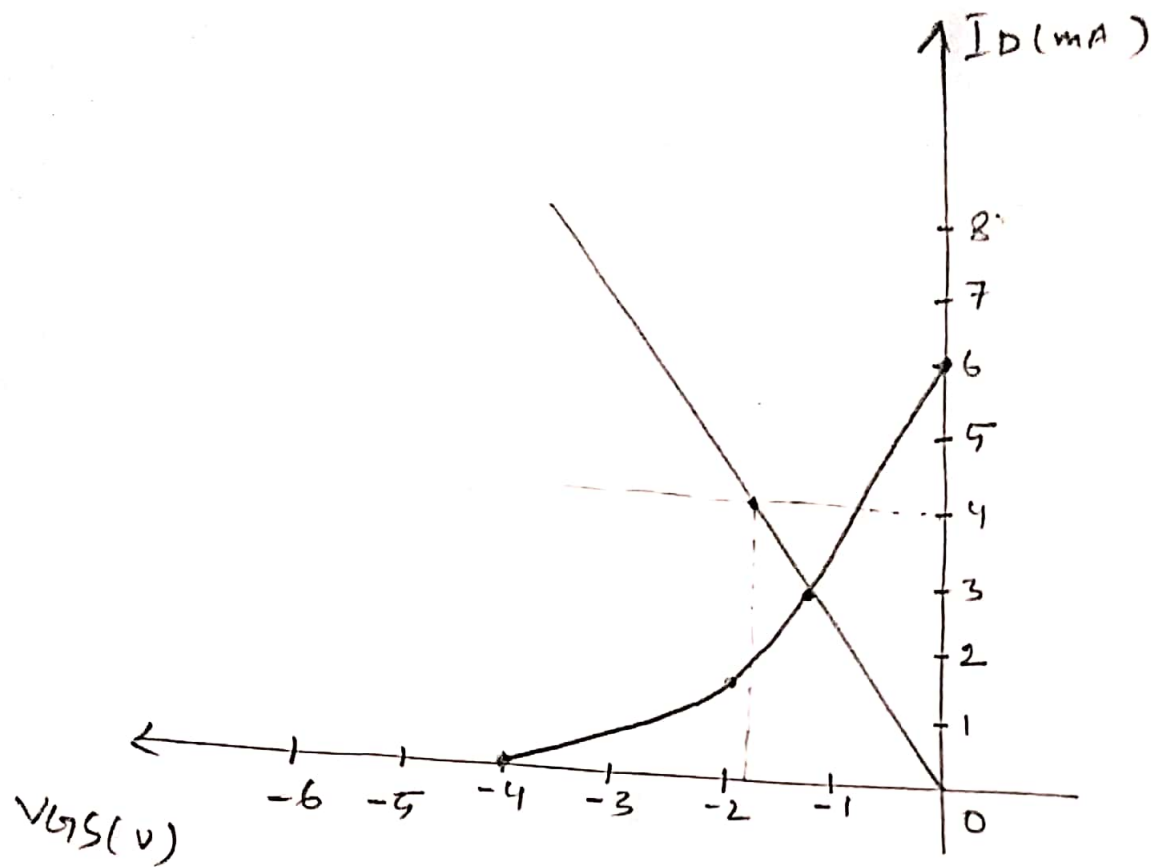
$$\begin{aligned}
 I_D &= 6 \left(1 - \frac{1}{-4} \right)^2 \\
 &= 6 \times (1.5625) \\
 &= 9.375 \text{ mA}
 \end{aligned}$$



Now eq ①

$$V_{GS} = -I_D (0.43)$$

$$I_D = 0, V_{GS} = 0$$

$$I_D = 4$$

$$V_{GS} = 1.72$$

(b) we know

$$V_{DS} = V_D - V_S$$

$$V_D = V_{DS} + V_S$$

$$V_{GS} = -I_D$$

$$I_D = 0, V_{GS} = 0$$

$$I_D = 6 \text{ mA}$$

$$V_{GS} = -4 \text{ V}$$

From Graph \rightarrow

$$I_D = 4$$

$$V_{GS} = 1.72$$

$$V_{DS} = V_{DD} - I_D R_D - I_D R_S$$

$$= V_{DD} - I_D (R_D + R_S)$$

$$V_{DD} = (32 \pm 5)_{+10}$$

$$= 17.6$$

$$= 17.6 - 4 (1.2 + 0.43)$$

$$= 17.6 - 6.52$$

$$= 11.08$$

$$V_S = I_D \times R_S = 4 \times 0.43 = 1.72$$

$$V_D = V_{DS} + V_S$$


$$= 11.08 + (I_D \times R_S)$$

$$= 11.08 + (4 \times 0.43)$$

$$= 12.8$$

Ans.

Q-5

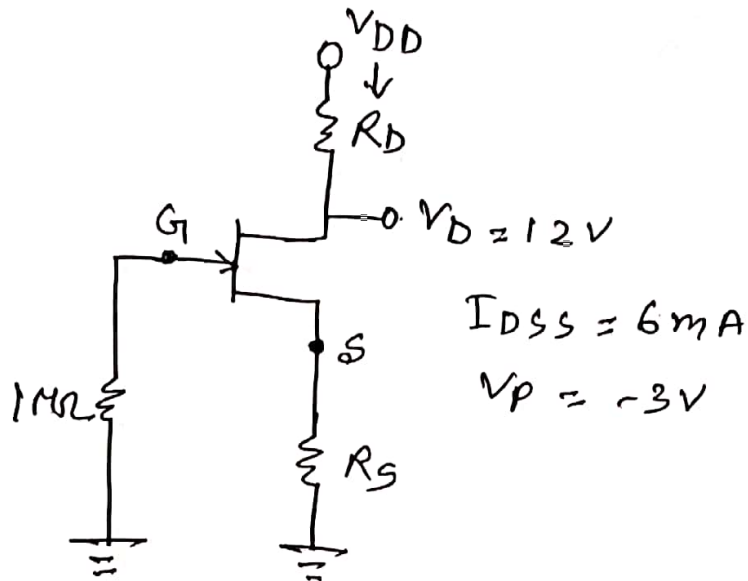

$$\begin{aligned}
 V_{DD} &= (I_D \div 5) + 15 \\
 &= (38 \div 5) + 15 \\
 &= 22.6
 \end{aligned}$$

$$\begin{aligned}
 I_{DQ} &= (I_D \div 20) mA \\
 &= 38 \div 20 \\
 &= 1.9
 \end{aligned}$$

① $V_{GS} = 0$

$$I_{DSS} = 6mA$$

② $V_{GS} = 0.3V_P$

$$= 0.3(-3) \quad I_D = 3mA$$

③ $V_{GS} = 0.5V_P$

$$= 0.5(-3)$$


$$= -1.5V$$

$$I_D = 1.5mA$$

②

$$V_{GS} = V_P$$
$$= -3$$

$$I_D = 0$$

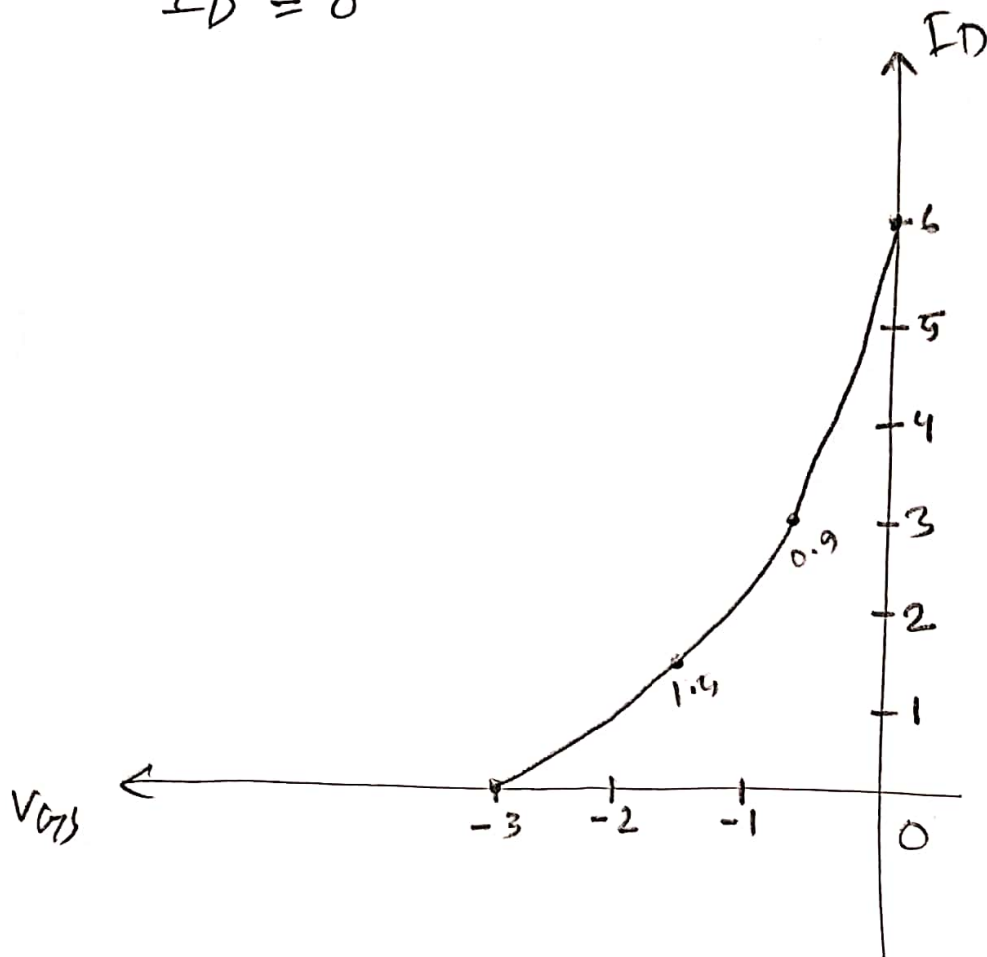

$$V_S = I_D R_S$$

$$R_S = \frac{V_S}{I_D} = \frac{12}{6} = 2 \text{ k}\Omega$$

$$V_{DS} = V_{DD} - I_D R_D$$

$$12 = 22.6 - (1.9 \times R_D)$$

$$R_D = 5.57 \text{ k}\Omega$$